

Files




NAND

00 → 1

01 → 1

10 → 1

11 → 0

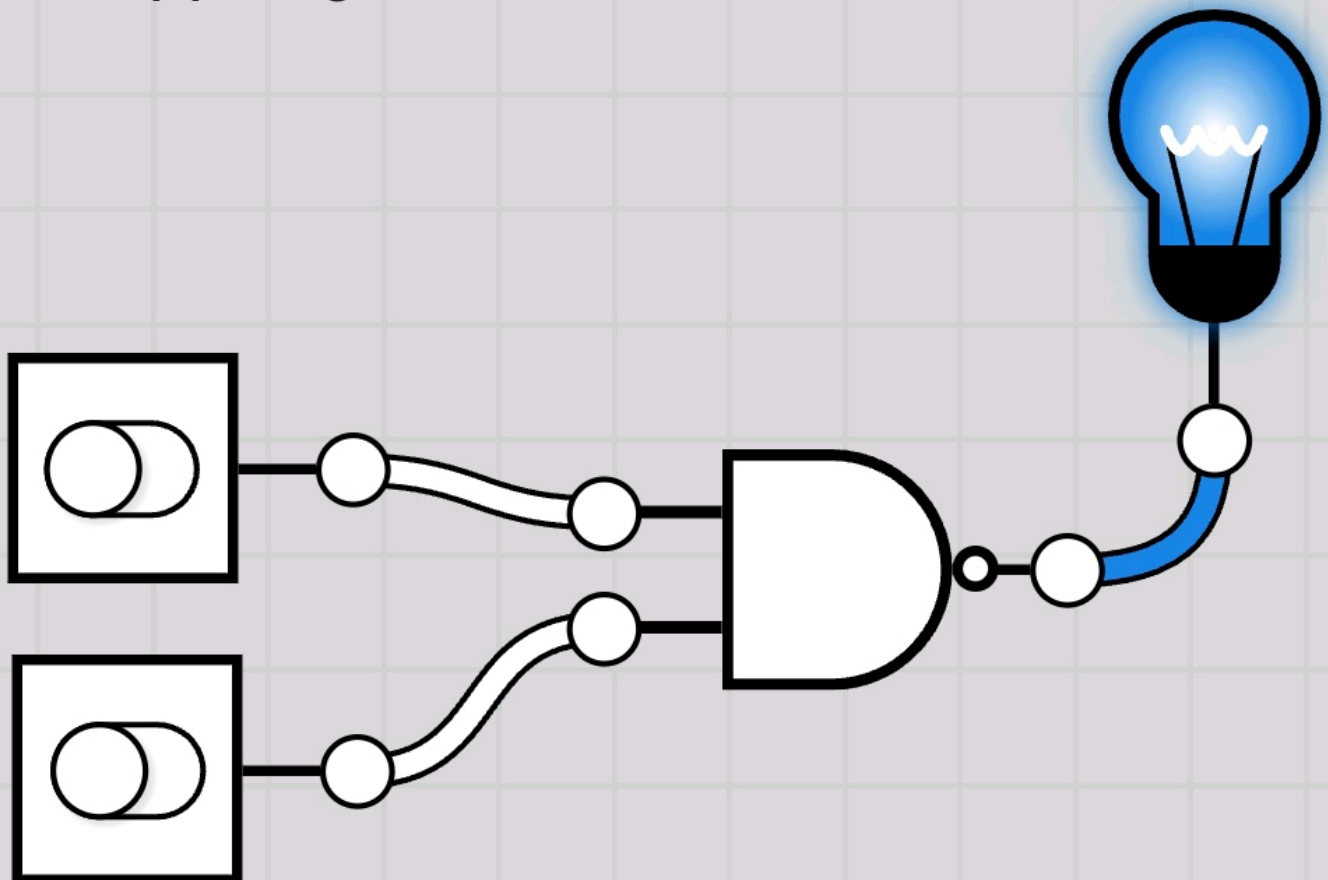

Files




AND

00 → 0

01 → 0

10 → 0

11 → 1

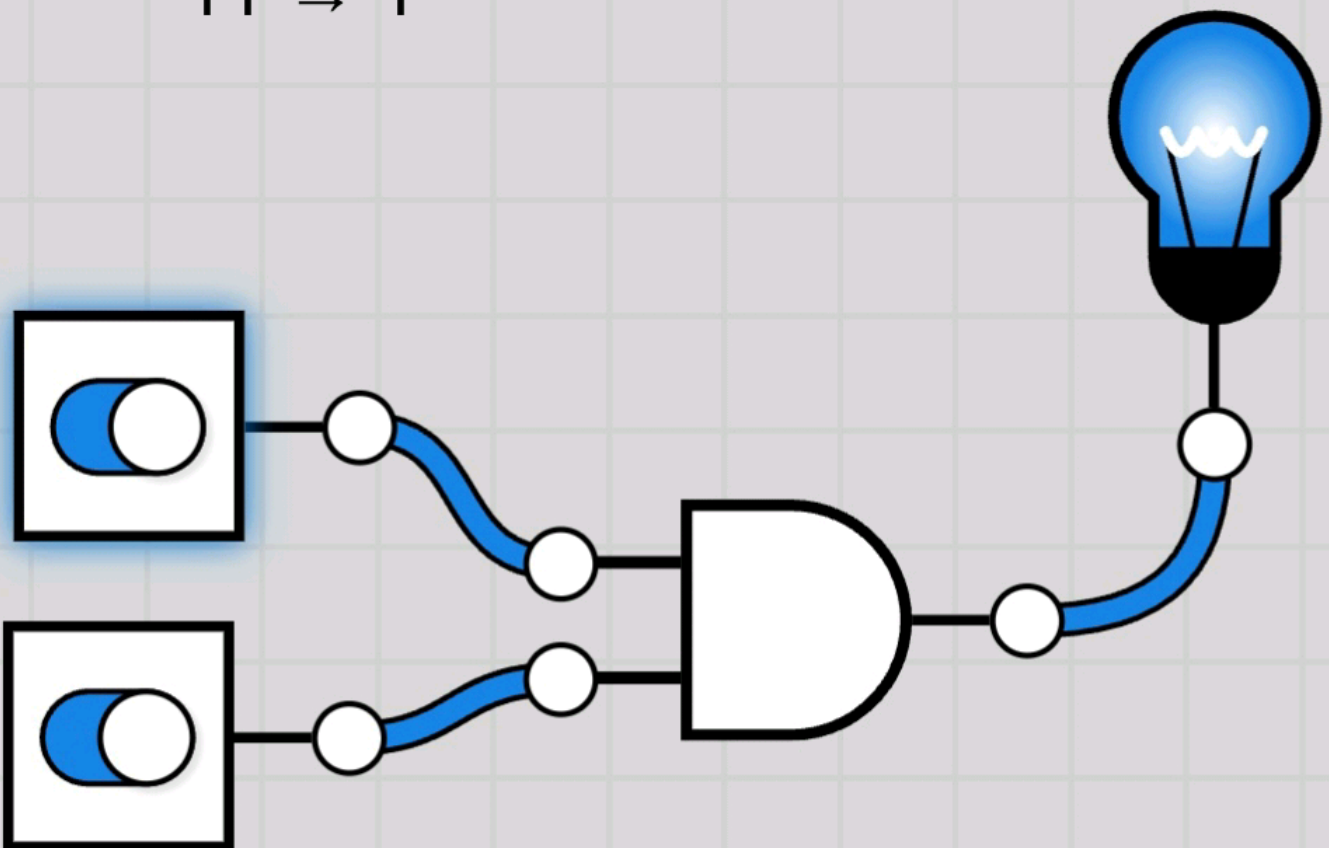

Files




NOR

00 → 1

01 → 0

10 → 0

11 → 0

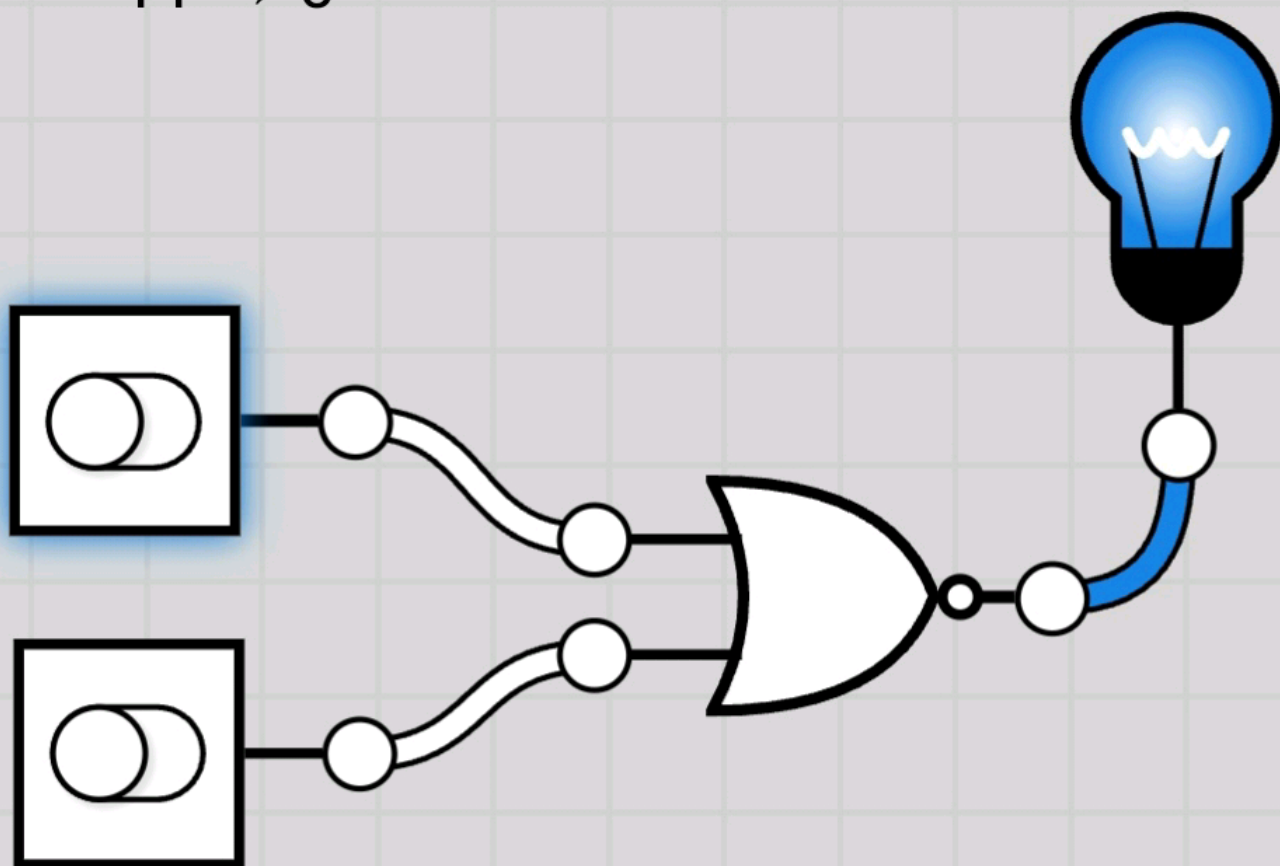

Files




OR

00 → 0

01 → 1

10 → 1

11 → 1

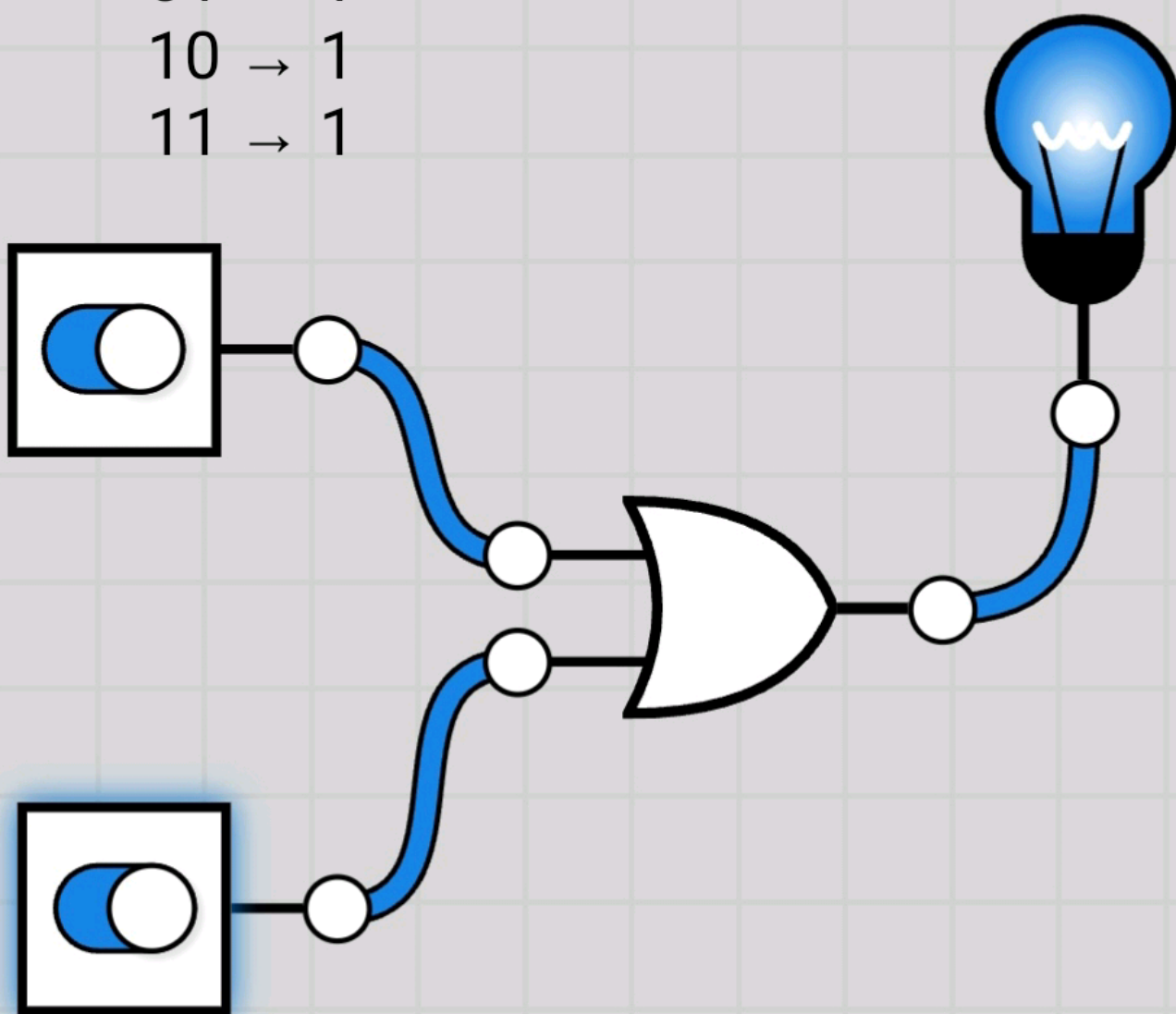




XOR

00 → 0

01 → 1

10 → 1

11 → 0

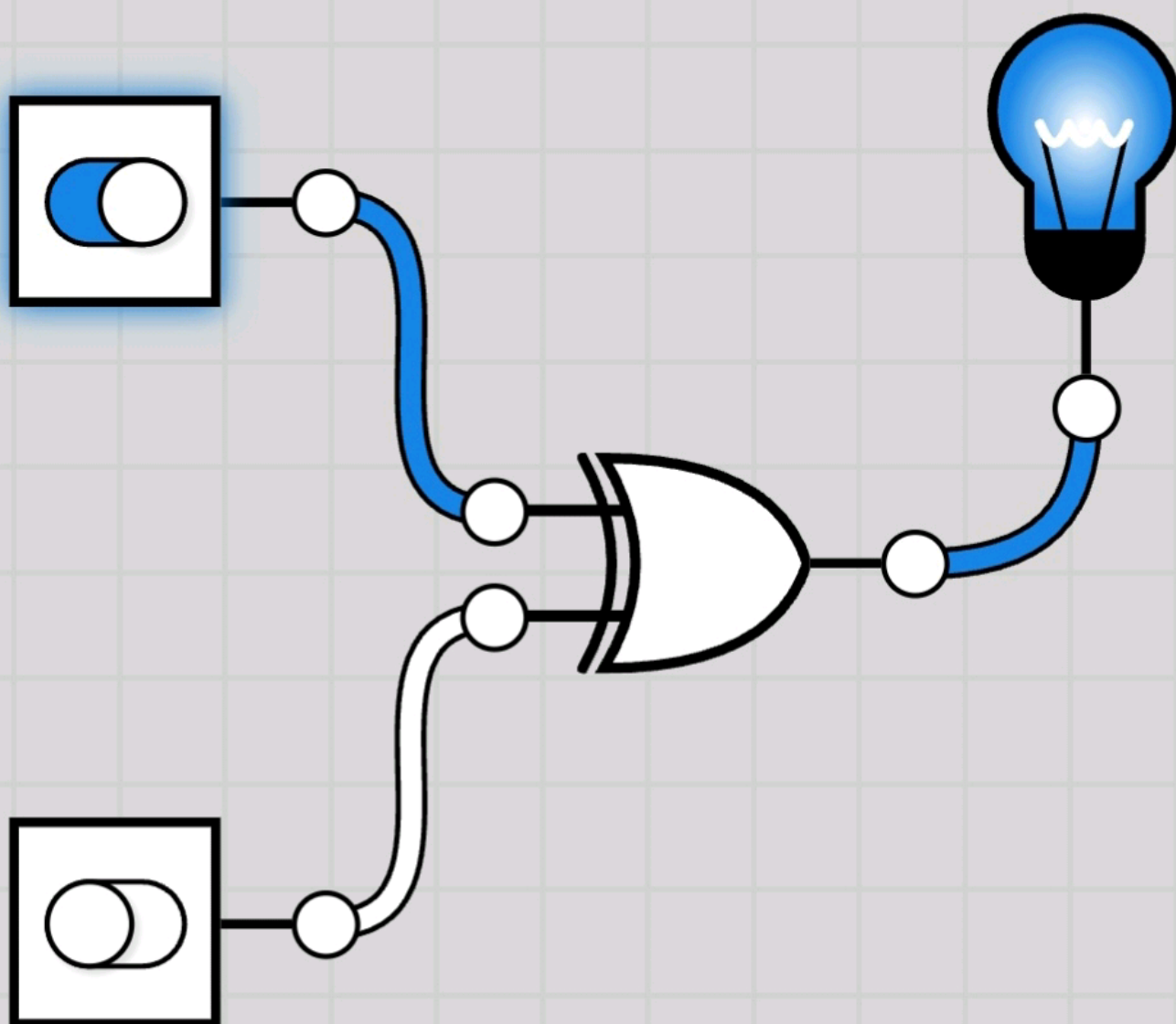


Files




NOT

0 $\rightarrow$ 1

1 $\rightarrow$ 0

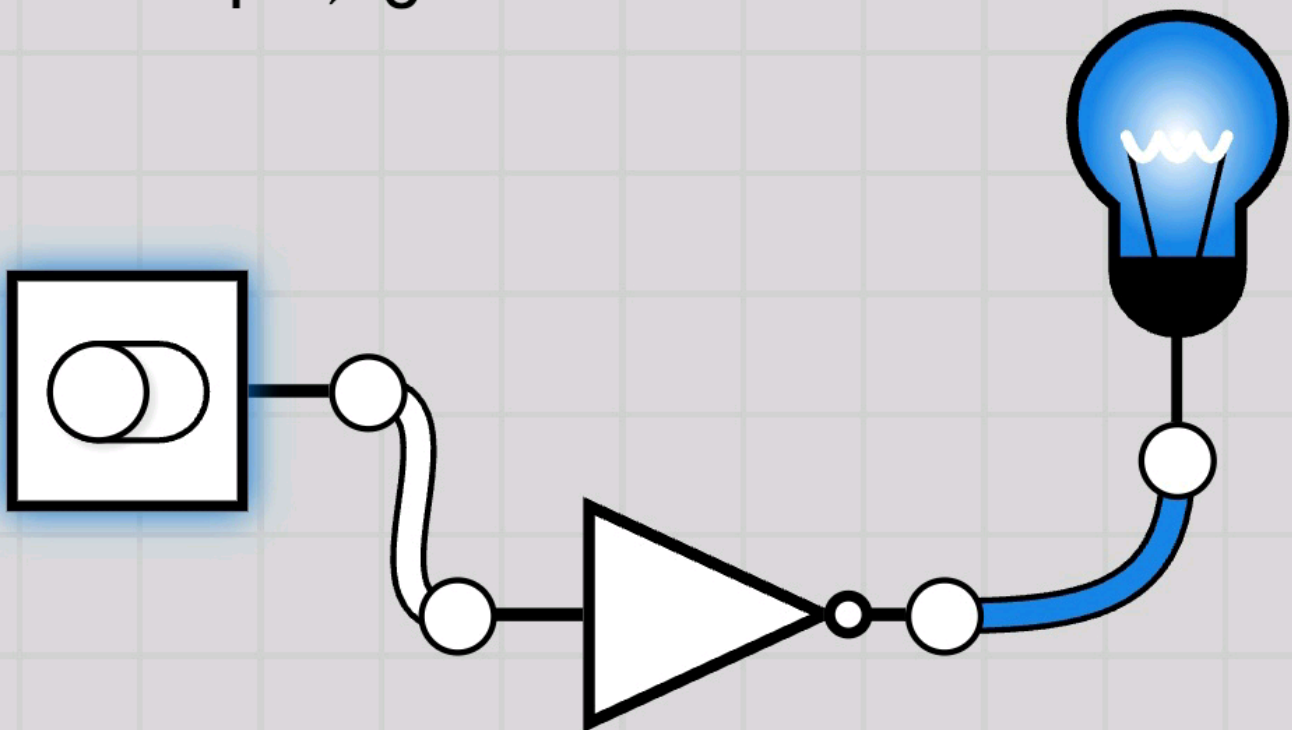

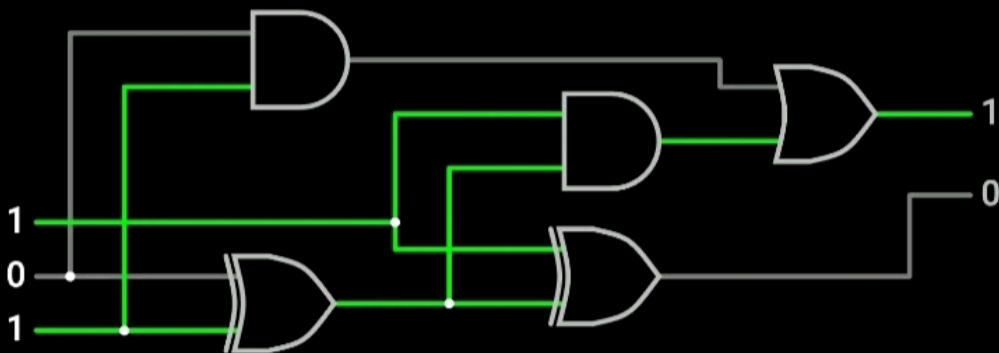File Edit Draw Scopes Options Tools Circuits



A	B	Cin	Sum (S)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

t = 12.58 ms
time step = 5 μ s

Reset

RUN / Stop

Simulation Speed



Current Speed



Power Brightness



Current Circuit:
Full Adder

File Edit Draw Scopes Options Tools Circuits

Reset


RUN / Stop

Simulation Speed

Current Speed

Power Brightness

Current Circuit:
Half Adder

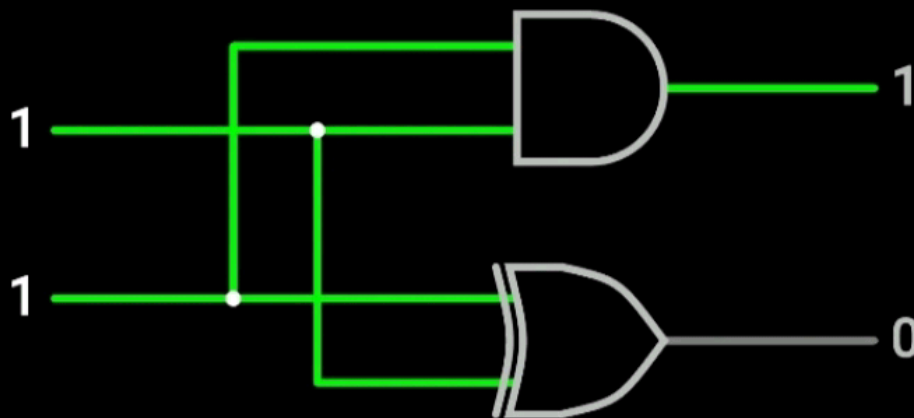

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

t = 101.425 ms
time step = 5 μ s